

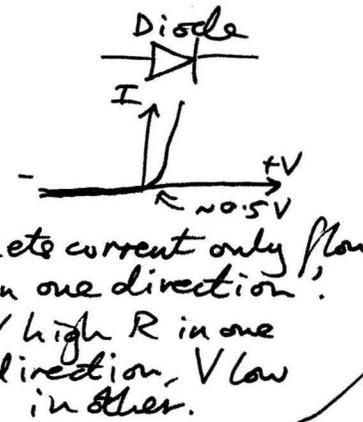
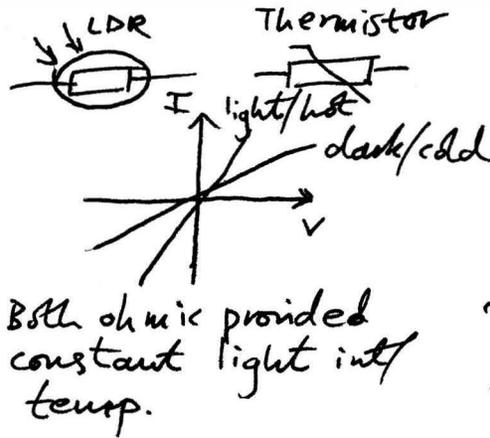
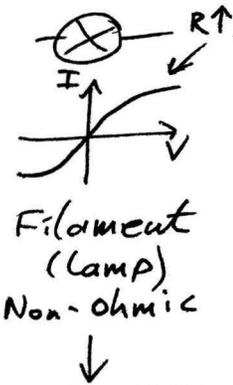
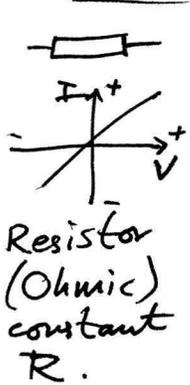


I-V characteristics

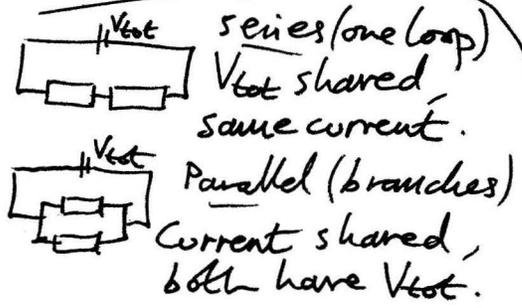

Power
 $P = IV = I^2R = \frac{V^2}{R}$

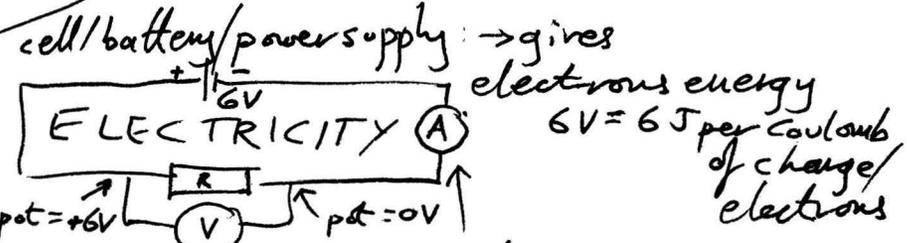When current increased, frequency of collisions of electrons with ions in lattice increases, making them vibrate more, increasing temp, making collisions even more likely, so $R \uparrow$.




Resistor converts electrical E into thermal, due to its Resistance (Symbol: R) (Unit: Ω)

Voltmeter goes 'across' component as it measures potential difference (p.d.) aka Voltage.

ammeter measures current (rate of flow of charge)
Symbol: I
Unit: A (amps)
 $I = \frac{Q}{t}$

- Whole \mathcal{E} or V from battery, must be 'used up' by circuit, so R gets all 6V.

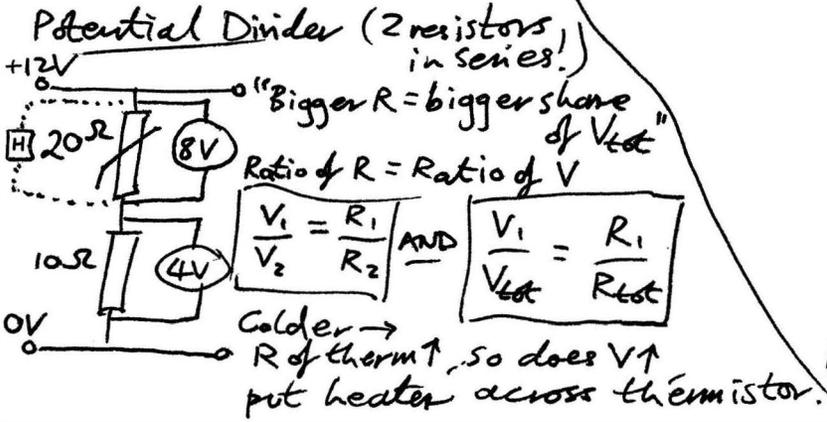$\frac{1}{R_{tot}} = \frac{1}{R_1} + \frac{1}{R_2}$
* If same, R_{tot} is half!



$V = \frac{E}{Q}$ $V = IR$
Ohm's Law