
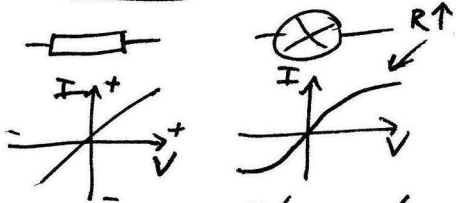


**I-V characteristics**

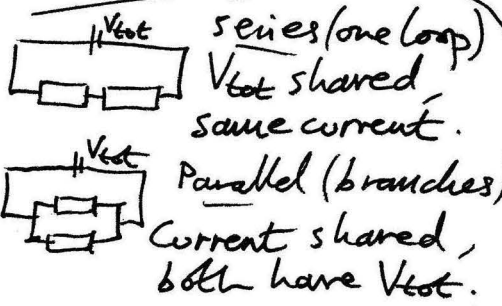


**Resistor (Ohmic) constant R.**  
**Filament (Lamp) Non-ohmic**


When current increased, frequency of collisions of electrons with ions in lattice increases, making them vibrate more, increasing temp, making collisions even more likely, so  $R \uparrow$ .



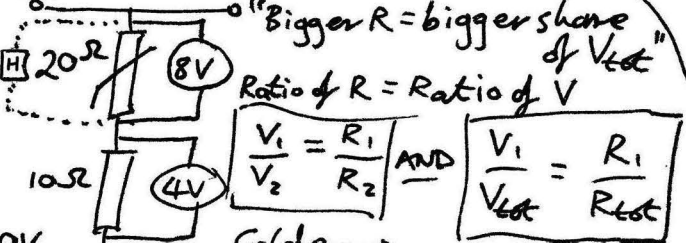
**Potential Divider (2 resistors in series)**



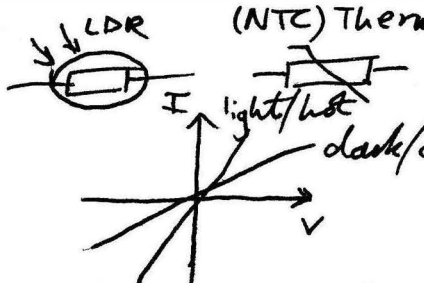Colder  $\rightarrow$   $R$  of therm  $\uparrow$ , so does  $V \uparrow$  put heater across thermistor.



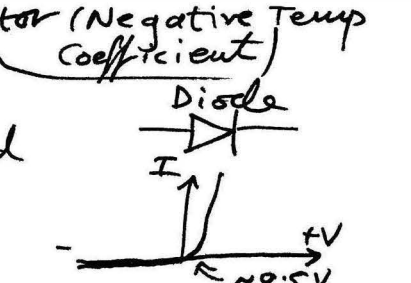
Both ohmic provided constant light/int, temp.  $E$  in 'shakes' electrons loose to conduct (conduction band),  $R \downarrow$ . ('Opposite to metal')



'Lets current only flow in one direction'.  $V$  high  $R$  in one direction,  $V$  low in other.

Resistor converts electrical  $E$  into thermal, due to its Resistance (Symbol:  $R$ ) (Unit:  $\Omega$ )

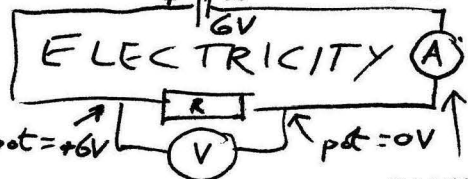cell/battery/power supply: provides emf ( $\epsilon$ ) (electromotive force)  $\rightarrow$  gives electrons energy



Voltmeter goes 'across' component as it measures potential difference (p.d.) aka Voltage.



ammeter measures current (rate of flow of charge)  
 Symbol:  $I$   
 Unit:  $A$  (amps)

$$I = \frac{Q}{t}$$

- Whole  $\epsilon$  or  $V$  from battery must be 'used up' by circuit, so  $R$  gets all 6V.

$$V = \frac{E}{Q} \quad V = IR \text{ (Ohm's Law)}$$

**Internal Resistance**

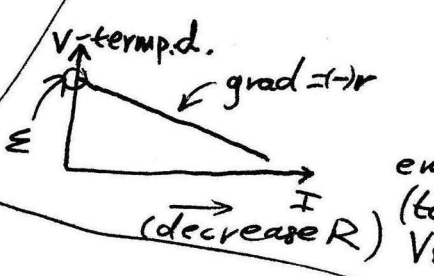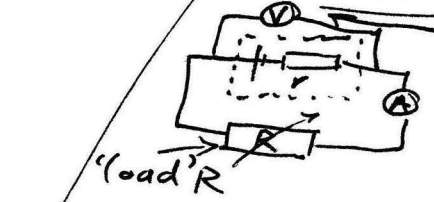

terminal p.d. ( $V$  available to circuit/load  $R$  after some of  $E$  lost)


$$\epsilon = IR + Ir$$

$\epsilon$  (total  $V_{supplied}$ )  
 $V$  (lost) in battery  
 $(E = V + Ir)$   
 $(E = I(R + r))$

**Power**  
 $P = IV = I^2R = \frac{V^2}{R}$

**Resistivity** ( $\rho$ )  
 $R = \frac{\rho L}{A}$

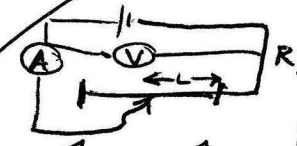Unit:  $\Omega m$   
 $\rho = \frac{RA}{L}$   
 $\rho = \text{grad} \times A$



diameter  $\times 2$ ,  $A \times 4$ ,  $\therefore R \downarrow \div 4$

**Kirchhoff's Laws:** 1st: charge is conserved at junctions  $\therefore e.g. I_1 = I_2 + I_3$

2nd: sum of  $E =$  sum of p.d. 'drops' in any closed loop.  
 $E = 3V$

$\frac{1}{R_{tot}} = \frac{1}{R_1} + \frac{1}{R_2}$   
 \* If same,  $R_{tot}$  is half!